

Roll No.

[illegible]

Total No. of Questions : 09

B.Tech.(Electrical Engineering) PT (Sem.-1)

CIRCUIT THEORY

Subject Code : BTEE-301

M.Code : 70971

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. **SECTION-A is COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION - B & C.** have **FOUR** questions each.
3. Attempt any **FIVE** questions from **SECTION B & C** carrying **EIGHT** marks each.
4. Select atleast **TWO** questions from **SECTION - B & C**.


SECTION-A

1. Answer briefly :


- What do you mean by doublet? Explain.
- State superposition theorem.
- Differentiate between time and frequency domain analysis.
- What do you mean by transfer function? Explain.
- What do you mean by propagation constant? Explain.
- Why network synthesis is required? Explain.
- Write down the disadvantages of constant-K filters.
- What do you mean by impulse response? Explain.
- What is characteristic impedance? Explain.
- Compare step and ramp signals.

SECTION-B

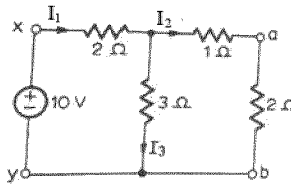2. Show the application of reciprocity theorem in the network shown below.




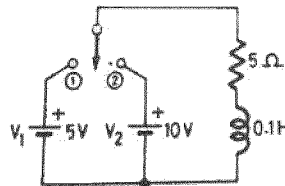3. Explain the concept of pole and zero in a network function and discuss its important features. Also discuss the restrictions on location of poles and zeros in driving point functions.
4. Design an m-derived T section low pass filter having cut-off frequency 7kHz, design impedance 600 ohm and frequency of infinite attenuation 10.5 kHz.
5. Obtain the expression for the current $i(t)$ when switch is moved from position 1 to position 2 at $t=0$.



SECTION-C

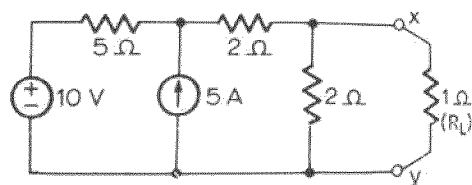6. What is a filter? What is its importance in circuit theory? Explain (in detail) the classification of filters.
7. Find the power loss in 1 ohm resistor using Norton's theorem and verify the result using Thevenin's theorem.



8. Design a low pass composite filter to operate with a design impedance of 500 ohms, $m=0.2$ and cut-off frequency = 2000Hz.
9. Discuss the following :
- Convolution theorem.
 - Foster forms by considering a suitable example.

NOTE : Disclosure of identity by writing mobile number or making passing request on any page of Answer sheet will lead to UMC against the Student.