Roll No.						Total No. of Pages: 0
						. otal itol ol i agoo i o

Total No. of Questions: 08

M.Tech. (Microelectronics) (Sem.-2)

## ANALOG AND MIXED SIGNAL DEVICE DESIGN

Subject Code: ME-810 M.Code: 38410

Time: 3 Hrs. Max. Marks: 100

## **INSTRUCTIONS TO CANDIDATES:**

- 1. Attempt any FIVE questions out of EIGHT question.
- 2. Each question carry TWENTY marks.
- 1. Explain the role of Analog Mixed signal in VLSI design.
- 2. a. Explain the operation of Sample and Hold circuit in Data converters.
  - b. Explain the basic cells of A to D converts.
- 3. a. Explain the basic operation of Dual slop ADC.
  - b. Explain the operation of Flash ADC and its advantages.
- 4. Why we use compensation approach in OP-Amp design and explain the Miller Compensation technique with suitable diagram?
- 5. Derive the expression of voltage gain and output resistance for an active-load MOS differential amplifier.
- 6. a. Explain the role of Decimation filter in Delta Sigma ADC.
  - b. Explain the operation of function generator.
- 7. a. Assume that a DAC uses a Switched capacitor non inverting amplifier with C1 = C2 and GB = 1 MHz. Find the conversion time of an 8-bit DAC if  $V_{ref}$  is IV.
  - b. Explain the role of Voltage controlled oscillator in PLL.
- 8. Short notes (**Any FOUR**):
  - a Phase detector
  - b. Switched Capacitor
  - c. Multipliers
  - d. Modulators
  - e. Charge pump PLL.

NOTE: Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.

1 | M-38410 (S9)-2745