

Total No. of Questions : 08

ANALOG DIGITAL & MIXED SIGNAL CMOS DESIGN

Subject Code : MTVL-103-18


M.Code : 76197

Max. Marks : 60

1. Attempt any FIVE questions out of EIGHT questions.

2.Each question carries TWELVE marks.

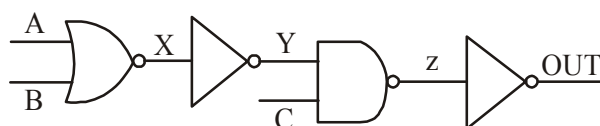
- Q.1 (a) Draw voltage transfer characteristics of CMOS inverter and derive expression for V_{IL} , V_{IH} , V_{OL} and V_{OH} .
- (b) Implement 4:1 MUX using pass transistor logic and transmission gate logic.
- Q.2 (a) Briefly explain cascaded domino CMOS logic circuit for high performance dynamic logic circuit.
- (b) For the circuit below, What are the activity factors of nodes X, Y, Z and OUT if $P(A=1) = P(B=1) = P(C=1) = 0.5$?



- Q.3 (a) Draw the circuit diagram for CMOS two-input NAND gates and explain its operation.
(b) Draw the stick diagram for CMOS two-input NOR gate.
- Q.4 (a) Design a CMOS clocked SR flip flop and explain its operation.
(b) Draw and explain the operation of C^2 MOS master slave positive edge triggered register.
- Q.5 (a) Why is emitter resistance R_E replaced by a constant current bias circuit in differential amplifier stage of an op-amp?
(b) An active-loaded MOS differential pair as shown in Fig. 2 is specified as follows :

$$\left(\frac{W}{L}\right)_n = 100, \left(\frac{W}{L}\right)_p = 200, \mu_n C_{ox} - 2\mu_p C_{ox} = 0.2 \text{ mA/V}^2, V_{An} = |V_{Ap}| = 20 \text{ V}, I = 0.8 \text{ mA}, R_{ss} = 25 \text{ k}\Omega.$$

Calculate G_m , R_0 , A_d , $|A_{cm}|$ and CMRR.

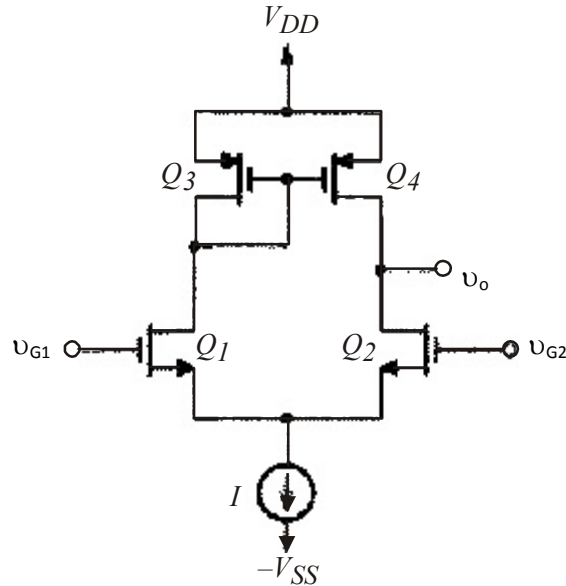

- Q.6 (a) Draw a standard cascode current sink circuit and explain its operation and output characteristics.
- (b) Explain why the Gilbert cell can operate as an analog voltage multiplier.
- Q.7 (a) Explain the principle of Miller Compensation of two stage op-amp.
- (b) Design an op-amp with ideal op-amp characteristics. Explain the steps, conditions and requirements to design an op-amp.
- Q.8 Write short notes on any **two** of the following :
- (a) FinFET
 - (b) Non-bistable sequential circuit
 - (c) Speed and power dissipation in dynamic logic

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.