

Roll No. 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 07

**BCA (Sem.-2)**  
**DIGITAL LOGIC AND CIRCUIT DESIGN**  
Subject Code : BC-205  
Paper ID : [B0209]

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTIONS TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and students have to attempt any FOUR questions.

**SECTION-A**

1. Answer briefly ;

- a) Write a short note on ASCII code.
- b) What is Universal Gate?
- c) Difference between combinational and sequential circuits.
- d) How SOP is used to solve Boolean expression?
- e) Draw a 4\* 1 multiplexer.
- f) What are the applications of shift registers?
- g) Give truth table of D Flip flop.
- h) What are decoders?
- i) Draw programmable counter.
- j) List the application of flip flops.

## SECTION-B

- Q2 What is Number System? Explain 1's complement and 2's complement with example.
- Q3 What are Karnaugh Maps? How they are used to simplify the equations?
- Q4 Explain Binary adder and subtracter with block diagram.
- Q5 What is race condition in JK flip flop? How it can be removed?
- Q6 What is Boolean Algebra? Discuss the role of De Morgan's Theorems in solving the Boolean Algebra.
- Q7 What is error detection and what are its methods? Explain any one in detail.