

Roll No.

Total No. of Pages : 02

Total No. of Questions : 07

B.Sc. (IT) (2019 Batch) (Sem.-1)
COMPUTER SYSTEM ARCHITECTURE

Subject Code : UGCA-1908

M.Code : 76954

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and students have to attempt any FOUR questions.

SECTION-A

1. Write briefly :

- a. How NAND gate is used as Universal Gate?
- b. What is SOP form?
- c. What are Karnaugh Maps?
- d. Draw a 4*1 multiplexer.
- e. Write the truth table of D Flip Flop.
- f. Write a short note on decoder.
- g. Discuss Von Neumann Architecture.
- h. What is Latch?
- i. Give example of Instruction format.
- j. What is use of registers?

SECTION-B

2. What are the applications of Logic Gates? Give some examples.
3. Design a combination circuits for a full adder and explain it in detail.
4. What is race condition in JK Flip Flop? How it can be removed?
5. Explain the differences between RISC and CISC architectures with examples?
6. Discuss the register transfer and micro operation in computer organization.
7. Give the introduction and operations of common Bus System in Computer organization.

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.