



### SECTION-B

2. State and explain Coulomb's law.
3. State Ohm's law and explain it with the help of a suitable example.
4. Explain color coding of a resistor. What will be color code of a resistor having value  $100000 \pm 5\%$  ohm?
5. Discuss different types of capacitors. How are capacitors tested?
6. Draw Hysteresis (B-H) curve. Where is it used?

### SECTION-C

7. A series-connected R-L-C circuit, supplied with an ac voltage source of 230V (rms) and 50-Hz, has  $R = 4\Omega$ ,  $L = 25\text{mH}$  and  $C = 4\mu\text{F}$ . Determine source current and power factor.
8. Discuss basic working principle of a transformer. A 200kVA, 250/500-V transformer delivers power at full load and at 0.8 p.f. lagging. The losses of the transformer at full load are 500W. Calculate its efficiency.
9. Write short notes on operation, uses and applications of filters.

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**