

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

**B.Tech.(Electrical & Electronics Engg./Electronics & Electrical)
(2018 Batch) (Sem.-3)**

ELECTRICAL CIRCUIT ANALYSIS

Subject Code : BTEEE-301-18

M.Code : 76463

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

SECTION-A

1. Write briefly :

- a. Discuss the significance of compensation theorem.
- b. State Norton theorem.
- c. What do you mean by time constant? Discuss its effect on the circuit performance.
- d. Why Laplace transform is used in circuit analysis? Discuss.
- e. What do you mean by complex power? Discuss.
- f. Define the coefficient of coupling.
- g. What is characteristic impedance? Explain.
- h. Write down the disadvantages of constant-k filters.
- i. What do you mean by driving point impedance? Explain.
- j. Discuss the importance of frequency response.

SECTION-B

2. State and prove (by considering an example) maximum power transfer theorem as applied to ac circuits.
3. In a RC series circuit $R = 1 \text{ ohm}$ and $C = 0.5 \text{ farad}$. Find the current $i(t)$ if an exponential voltage $v(t) = 10e^{-t}$ is suddenly applied at $t = 0$. Assume no initial charge in the capacitor.

4. Find the second Cauer form of the function $Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$

5. Two 2 port networks A and B are connected in parallel.

The Y parameters of the network A are

$$Y_{11a} = 1 \text{ mho}, Y_{12a} = -2 \text{ mho}, Y_{21a} = 2 \text{ mho}, Y_{22a} = 5 \text{ mho}$$

The Y parameters of the network B are

$$Y_{11b} = -1.5 \text{ mho}, Y_{12b} = -1 \text{ mho}, Y_{21b} = 2 \text{ mho}, Y_{22b} = 2 \text{ mho}$$

Determine the Z parameters of the resultant network.

6. A series circuit consists of a resistance of 4Ω , an inductance of 500mH and a variable capacitance connected across a 100V , 50Hz supply. Calculate the capacitance require to produce a series resonance condition, and the voltages generated across both the inductor and the capacitor at the point of resonance.

SECTION-C

7. Using the principle of superposition, calculate the voltage $V_2(t)$ in the figure. Assume $R_1=R_2= 1 \text{ ohm}$, $R_3=0.5 \text{ ohm}$, $C=2 \text{ F}$, $\beta=2$, $\alpha=1$ and $i(t)=\sin t$, $v(t) = t$.

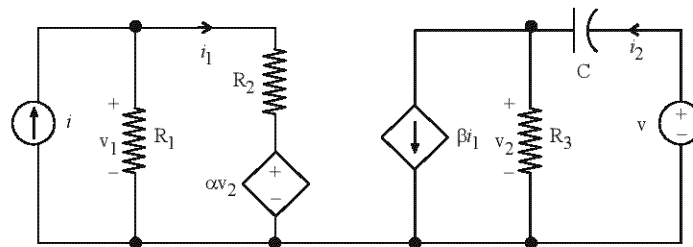


FIG.1

8. a. Determine the stability of the system using the Routh-Hurwitz criterion for the given polynomial $F(s) = 2S^5 + 2S^4 + 4S^3 + 4S^2 + 22S + 20$
- b. Discuss the concept of poles and zeros in a network function. Also discuss the restrictions on the location of poles and zeros in the driving point functions.
9. Discuss the following in detail :
- a. Filters and their classification
- b. Design of m-derived filters

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.